

Positive Real Function (PRF)

expression written now design $\sin(\omega)$, ~~not PRF~~ ~~g348~~ 1

A function $F(s)$ is said to be positive real function (PRF) if and only if the following conditions satisfied.
(Necessary and sufficient conditions for PRF)

1. All the poles and zeros must lie on the left half of s-plane.
2. The poles and zeros may lie on the jw but the residue must be positive.
(partial fraction and their real constants \rightarrow Residue)
3. $R_{\text{real}}(M_1, M_2 - N_1, M_2 > 0)$ for all ω

where

M_1 = even part of numerator (num)

N_1 = odd " " "

M_2 = even part of denominator (den)

N_2 = odd " " " "

* Properties of a PRF

- ① If a function $F(s)$ is PRF then its $\frac{1}{s} F(s)$ is also PRF.
- ② The sum of two PRFs is also a PRF.
- ③ The subtraction of two PRFs is also a PRF.
- ④ The coefficients of the numerator and denominators of the function should be positive.
- ⑤ The poles are simple and may lie on jw axis with positive residue.

- (6) The difference of highest powers of numerator and denominator should not exceed than unity (1).
- (7) The difference of lowest powers of numerator and denominator should not exceed than unity (1).

Example

$$H(s) = \frac{s^2 + 9s + 3}{s^2 + 7s + 9} \quad \text{check for positive realness (PRF)}$$

- Sol
- a) All the coefficients of the numerator and denominator are positive.
 - b) denominator $\rightarrow -7 \pm \sqrt{7^2 - 4 \times 1 \times 9}$
 $= \pm 2\sqrt{-1}$ { of imaginary poles }
 $= \pm 2i$ { partial fraction finding }
 - c) $M_1 M_2 = N_1 N_2$ { no residue test necessary }
 $M_1 M_2 = N_1 N_2$ { residues which must have sum }
 $m_1 = s^2 + 3$
 $n_1 = 9s$

$$\text{even part of numerator } m_1 = s^2 + 3$$

$$\text{odd } n_1 = 9s$$

$$\text{even denominator } M_2 = s^2 + 9$$

$$M_2 = 7s + 2$$

$$M_1 M_2 = N_1 N_2$$

$$= (s^2 + 3)(s^2 + 9) - 9s * 7s$$

$$= s^4 + 12s^2 + 27 - 63s^2$$

$$= s^4 - 51s^2 + 27$$

$$\text{put } s = j\omega$$

$$= (j\omega)^4 - 51(j\omega)^2 + 27$$

$$\text{Real} = \omega^4 + 51\omega^2 + 27 \quad \text{For all } \omega = \text{re } \omega + \text{im } \omega$$

$$\omega^4 + 51\omega^2 + 27 > 0.$$

method ②. (if power of denominator > 2 check condition Hurwitz.)
Page

d) Power difference is lesser than 1.

Hence,

The given function is PRF.

$$g) H(s) = \frac{s^3 + 5s^2 + 9s + 3}{s^3 + 9s^2 + 7s + 9} \quad \text{check for PRF.}$$

so

a) All the coefficients of numerator & denominator are positive.

b) (always denominator.)

The denominator polynomial is Hurwitz or not?

$$\text{even part} = 4s^2 + 9$$

$$\text{odd part} = s^3 + 7s$$

Continue division on fraction.

$$9s^2 + 9 \left(\begin{array}{r} s \\ - \end{array} \right)$$
$$s^3 + 7s \left(\begin{array}{r} s \\ - \end{array} \right)$$
$$- \quad - \quad \overline{9s}$$

$$\frac{19s}{9} \left(\begin{array}{r} 9s^2 + 9 \\ - \end{array} \right) \left(\begin{array}{r} 9s \times 4 \\ - \end{array} \right)$$
$$9s^2 + 9$$

$$9 \left(\begin{array}{r} 19s \\ - \end{array} \right) \left(\begin{array}{r} 19s \\ - \end{array} \right) \left(\begin{array}{r} 19s \\ - \end{array} \right)$$

In the given continue fraction

all quotients are positive

so the given polynomial is

Hurwitz.

{ no need to check }
{ imaginary }

c) even numerator $M_1 = s^5 + 3$

odd denominator $N_1 = s^3 + 9s$

even denominator $M_2 = 4s^2 + 9$

odd $N_2 = s^5 + 7s$

now, $M_1 M_2 - N_1 N_2$

$$= (s^5 + 3)(4s^2 + 9) - (s^3 + 9s)(s^5 + 7s)$$

$$= 20s^7 + 4s^5 + 12s^2 + 27 - (s^8 + 7s^6 + 9s^7 + 63s^2)$$

$$= 20s^7 + 5s^5 + 27 - s^8 - 16s^6 - 63s^2$$

$$= -s^8 + 4s^7 - 6s^6 + 27$$

put $s = j\omega$

$$= -(j\omega)^8 + 4(j\omega)^7 - 6(j\omega)^6 + 27$$

$$= \omega^8 + 4\omega^7 + 6\omega^6 + 27$$

$$\geq 0$$

for all ω .

d) power difference is less than 1.

Hence, given function is positive real function.

1 → the coefficient

2 → the residue, poles lie in left half plane

3 → $M_1 M_2 - N_1 N_2 > 0$

real axis.



Q.

$$H(s) = \frac{(s+1)(s+3)}{(s+2)(s+4)} = \frac{s^2 + 4s + 3}{s^2 + 6s + 8}$$

a) All the coefficients are +ve.

b) $s+2=0 \Rightarrow s=-2$

$s+4=0 \Rightarrow s=-4$

All poles lie on -ve real axis.

No residue or Hurwitz test required.

c) $M_1, M_2 - N_1, N_2$

$$= (s^2 + 3)(s^2 + 8) - 4s \times 6s$$

$$= s^4 + 11s^2 + 24 - 24s^2$$

$$= s^4 - 13s^2 + 24$$

put $s=j\omega$

$$= (\omega)^4 - 13(\omega)^2 + 24$$

$$= \omega^4 + 13\omega^2 + 24$$

$$\geq 0$$

for all ω .

d) power difference < 1 .

Hence given function is PRF.

Q. $Z(s) = \frac{s(s^2+2)}{(s^2+1)(s^2+3)}$ check PRF!

$$= \frac{s^3 + 2s}{s^4 + 4s^2 + 3}$$

a) all coefficients are +ve.

b) poles are $s^2+1=0$ / $s^2+3=0$
 $s^2 = \pm j\omega$ / $s = \pm j\sqrt{3}$

The poles are on Jw axis, so residue test is mandatory.

$$\frac{s(s^2+2)}{(s^2+1)(s^2+3)} = \frac{As+B}{s^2+1} + \frac{Cs+D}{s^2+3}$$

a) $s^3 + 2s = (As+B)(s^2+3) + (Cs+D)(s^2+1)$
 $= As^3 + 3As + Bs^2 + 3B + Cs^3 + Cs + Ds^2 + D$

$$A+C=1 \Rightarrow A=1-C$$

$$B+D=0 \Rightarrow B=-D$$

$$3A+C=2 \Rightarrow 3(1-C)+C=2$$

$$3B+D=0 \Rightarrow 3(-D)+D=0$$

$$-3D+D=0 \Rightarrow -2D=0$$

$$D=0$$

$$B=0$$

$$A=1-\frac{1}{2}$$

$$= \frac{1}{2}$$

Here all residues are +ve.

c) $M_1 M_2 - M_1 N_2$

$$= 2s(s^2 + 2s^2 + 3)^2 - s^3$$

$$= 2s^5 + 8s^3 + 6s - s^3$$

$$M_1 = 0$$

$$M_1 = s^3 + 2s$$

$$M_2 = s^2 + 2s^2 + 3$$

$$N_2 = 0$$

$$\therefore M_1 M_2 - M_1 N_2 = 0 \geq 0 \quad \text{for all } \omega.$$

d) power difference $= 1$ for highest as well as lowest.

Hence the given function is PRF.

Q.

Show that the given function is positive real.

$$q(s) = \frac{2s^2 + 2s + 1}{s^3 + 2s^2 + s + 2}$$

$$= \frac{2s^2 + 2s + 1}{s^2(s+2) + (s+2)}$$

$$= \frac{2s^2 + 2s + 1}{(s^2 + 1)(s + 2)}$$

a) all the coefficients are +ve.

b)

$$s^2 + 1 = 0 \Rightarrow s = \pm j\omega$$

residue test is required.

$$\frac{2s^2 + 2s + 1}{(s^2+1)(s+2)} = \frac{A}{s+2} + \frac{Bs+C}{s^2+1}$$

$$2s^2 + 2s + 1 = As^2 + A + Bs^2 + 2Bs + Cs + 2C$$

$$A + B = 2 \Rightarrow A = 2 - B = 2 - \frac{5}{6} \Rightarrow \boxed{A=1}$$

$$2B + C = 2 \Rightarrow C = 2 - 2B$$

$$A + 2C = 1$$

$$\Rightarrow 2 - B + ?(2 - 2B) = 1$$

$$2 - B + 2 - 4B = 1$$

$$-5B = -5$$

$$B = \boxed{1}$$

All the residues are true.

$$\text{c) } M_1 = 2s^2 + 1 \quad N_1 = 2s \\ M_2 = 2s^2 + 2 \quad N_2 = s^3 + s$$

$$M_1 M_2 - N_1 N_2 = (2s^2 + 1)(2s^2 + 2) - 2s(s^3 + s) \\ = 4s^4 + 6s^2 + 2 - 2s^4 - 2s^2 \\ = 2s^4 + 4s^2 + 2$$

$$\text{put } s = j\omega$$

$$= 2(j\omega)^4 + 4(j\omega)^2 + 2$$

$$= 2\omega^4 - 4\omega^2 + 2$$

$$> 0$$

for all ω .

d) power difference = 1.

Hence, given function is PRF.

Synthesis:

designing networks from the given immittance function \rightarrow impedance + admittance.

$$\text{Immittance} = \text{Impedance} + \text{Admittance}$$

LC, RCI, RL.

Design methods (model)Foster method (partial fraction)

↓
1st Foster
method
(impedance)

↓
Foster IInd
method
(admittance)

Cauer method (continued fraction)

↓
Cauer I
form.
↓
Cauer II
form.

* LC network.

- properties of LC immittance function

- (i) $Z_{LC}(s) \text{ or } Y_{LC}(s)$ is the ratio of odd to even or even to odd polynomials.
- (ii) The poles and zeros are simple and lie on $j\omega$ axis.
- (iii) The poles and zeros interlace on the $j\omega$ -axis
→ alternate. ($0 \times 0 \times$)
- (iv) The highest powers of numerator and denominator must differ by unit (1); the lowest power also differ by unity (1).
- (v) There must be either a zero or pole at the origin and infinity.

Foster I form for LC network (Impedance and find ω_0)


Do partial fraction of the given impedance function.

$$\text{Qd, } Z(s) = k_0 s + \frac{k_1 s}{s^2 + \omega_1^2} + \frac{k_2 s}{s^2 + \omega_2^2} + \dots + \frac{1}{k_{00} s}$$

be the result after partial fraction.

Realize into foster I form. $L_1 = \frac{k_1}{\omega_1^2}, L_2 = \frac{k_2}{\omega_2^2}$ } equivalent circuit

(series form)

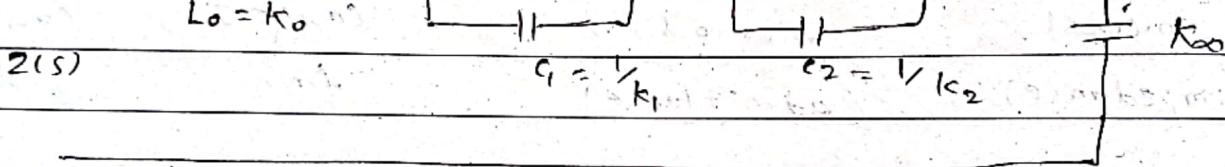


$$L \rightarrow Ls \quad LC \rightarrow \frac{ks}{s^2 + \omega^2}; L = \frac{1}{\omega}, C = \frac{1}{k}$$

Foster II form (Form admittance)

Do partial fraction of admittance function.

$$\text{Qd, } Y(s) = k_0 s + \frac{k_1 s}{s^2 + \omega_1^2} + \frac{k_2 s}{s^2 + \omega_2^2} + \frac{k_3 s}{s^2 + \omega_3^2} + \dots + \frac{1}{k_{00} s}$$


(parallel form)

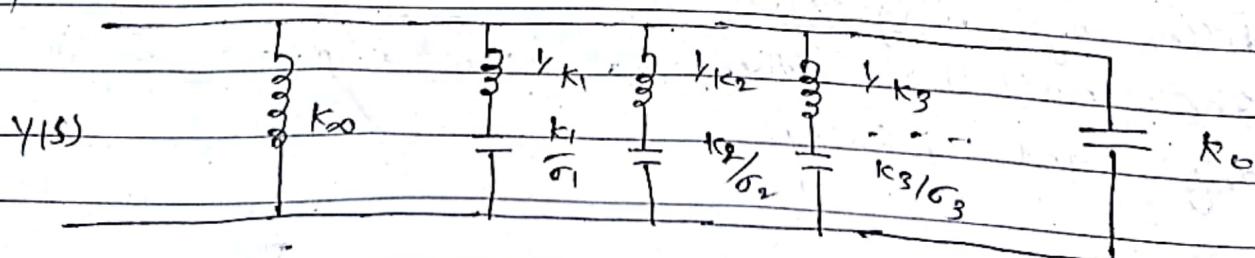


General foster II form for LC ω .

Foster I & II are L & C circuit value of ω
at first opposite $\frac{1}{\omega}$,
capacitor at inductor &
inductor at capacitor in $\frac{1}{\omega}$.

H. Cauer I form

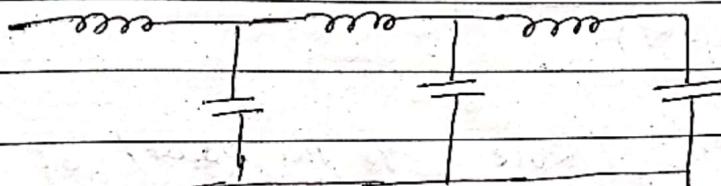

H. Cauer II form

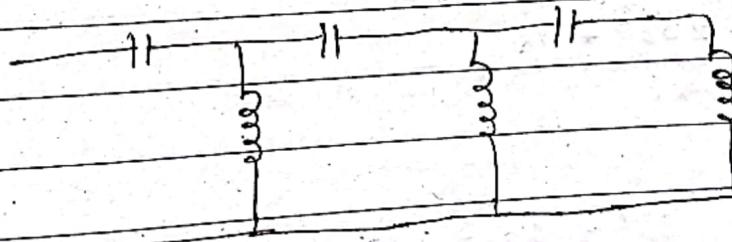

quotient $\frac{1}{\omega}$ of element $\frac{1}{C}$
is $\frac{1}{R}$ w.r.t |

Q. obtain the Foster I and II form of the LC impedance function.

$$Z(s) = \frac{2(s^2+1)(s^2+9)}{s(s^2+\alpha)}$$

Sol:

For Foster I form.

$$Z(s) = \frac{2(s^2+1)(s^2+9)}{s(s^2+\alpha)}$$

Partial fraction: (Rule - If the power of denominator is greater than numerator, only otherwise divide by actual division)

$$\frac{2(s^2+20s^2+9)}{s^3+9s}$$

$$= \frac{2s^2 + 20s^2 + 18}{s^3 + 9s}$$

$$\begin{array}{r} 2s^2 + 20s^2 + 18 \\ \hline 2s^2 + 8s^2 \\ \hline 12s^2 + 18 \end{array}$$

$$Z(s) = \frac{12s^2 + 18}{2s + \frac{s^3 + 9s}{s^2 + 4s}}$$

$$\frac{12s^2 + 18}{s(s^2 + 9)} = \frac{A}{s} + \frac{Bs + C}{s^2 + 4s}$$

$$\frac{12s^2 + 18}{s(s^2 + 7)} = \frac{A(s^2 + 7) + s(5s + c)}{s(s^2 + 9)}$$

$$= As^2 + 9A + Bs^2 + Cs$$

$$as^2 + 18 = (A+B)s^2 + \dots$$

66

equating coefficients,

$$A+B=12 \Rightarrow B=12-9, \frac{1}{2}$$

$$c = 0$$

$$4A = 18$$

$$A = g_{\mu\nu}$$

$$2(s) = 2s + \frac{9_{1/2}}{s} + \frac{15_{1/2}s}{s^2 + x}$$

$\Rightarrow 15_{1/2} \rightarrow 15_{1/2} F$

Fig. Foster I form.

For Foster II forms:

$$Z(s) = \frac{2(s^2+1)(s^2+9)}{s(s^2+9)}$$

$$Y(s) = \frac{1}{Z(s)} = \frac{s(s^2+9)}{2(s^2+1)(s^2+9)} = \frac{0.5 s (s^2+9)}{(s^2+1)(s^2+9)}$$

Partial fraction.

$$\frac{0.5s(s^2+9)}{(s^2+1)(s^2+9)} = \frac{As+B}{s^2+1} + \frac{Cs+D}{s^2+9}$$

$$\frac{0.5s}{s^2 + 1} = \frac{(As + B)(s^2 + 9) + (Cs + D)(s^2 + 1)}{(s^2 + 1)(s^2 + 9)}$$

$$0.5s^3 + 2s = As^3 + 9As + 3s^2 + 9B + Cs^3 + Cs + Ds^2 + D$$

equating,

$$A+C=0.5 \quad \text{--- (1)} \quad 9A+C=2 \quad \text{--- (3)}$$

$$B+D=0 \quad \text{--- (2)} \quad 9B+D=0 \quad \text{--- (4)}$$

solving.

$$A = \frac{3}{16}, \quad C = \frac{5}{16}$$

$$B = 0, \quad D = 0$$

$$Y(s) = \frac{\frac{3}{16}s}{s^2+1} + \frac{\frac{5}{16}s}{s^2+9}$$

No inductor & capacitor only. all mixes.

Capacitor T-T ~~1~~ ~~5-5~~ 1

Inductor ~~2-2~~ ~~5-5~~ 1

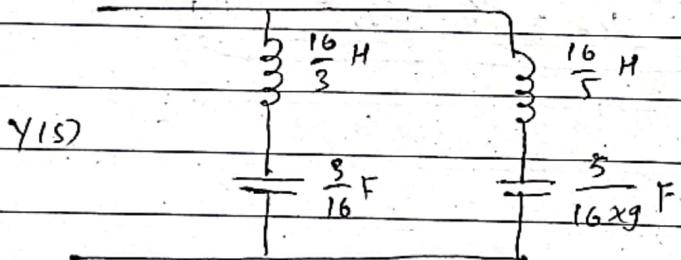


fig. Foster II form.

~~NT~~

2018/10/12

$$Y(s) = \frac{s(s^2+2)(s^2+9)}{(s^2+1)(s^2+3)}$$

$$= \frac{(s^3+2s)(s^2+9)}{s^4 + 4s^2 + 3}$$

For the given admittance function, realize for Foster IInd form of LC network.

$$s^5 + 6s^3 + 8s$$

$$s^4 + 9s^2 + 3$$

power in numerator > power in denominator

Now, by actual division

$$\begin{array}{r} s^4 + 9s^2 + 3 \\ \underline{-} s^5 + 6s^3 + 8s \\ \hline 2s^3 + 5s \end{array}$$

$$Y(s) = s + \frac{2s^3 + 5s}{s^4 + 9s^2 + 3}$$

$$Y(s) = s + \frac{2s^3 + 5s}{(s^2+1)(s^2+3)}$$

Now, partial fraction

$$\frac{2s^3 + 5s}{(s^2+1)(s^2+3)} = \frac{As+B}{s^2+1} + \frac{Cs+D}{s^2+3}$$

$$2s^3 + 5s = (As+B)(s^2+3) + (Cs+D)(s^2+1)$$

$$= As^3 + 3As + Bs^2 + Cs^3 + Cs +$$

$$Ds^2 + D$$

$$= (A+C)s^3 + (B+D)s^2 + (3A+C)s + D$$

Equation Coefficients,

$$A + C = 2$$

$$B + D = 0$$

$$3A + C = 5$$

$$2 = 0$$

$$B = 0$$

$$A = \frac{3}{2}$$

$$C = -\frac{1}{2}$$

Now

$$Y(s) = S + \frac{\frac{3}{2}s}{s^2+1} + \frac{\frac{1}{2}s}{s^2+3}$$

$$\tau$$


$$k_0 = 1$$

$$k_1 = \frac{3}{2}$$

$$k_2 = \frac{1}{2}$$

$$\sigma_1 = 1$$

$$\sigma_2 = 3$$

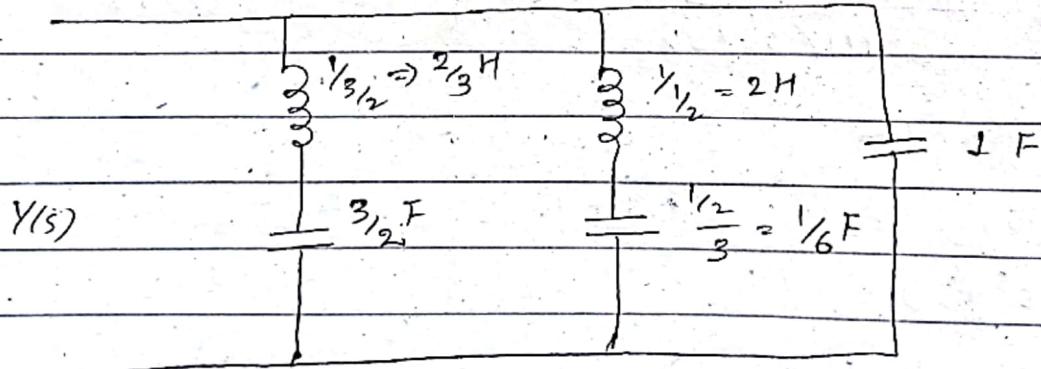

Q: obtain Cauer I form of the given impedance function.

$$Z(s) = \frac{2s^5 + 12s^3 + 16s^1}{s^7 + 9s^2 + 3}$$

Sol: For Cauer form, denominator highest power should be lesser. (always).

Rule: For Cauer I form, arrange the given polynomials in the descending order.

(continued fraction method are same \Rightarrow)

$$\begin{array}{c} s^7 + 9s^2 + 3 \\) 2s^5 + 12s^3 + 16s^1 \\ - 2s^5 - 8s^3 - 6s^1 \\ \hline 4s^3 + 10s^1 \end{array} \quad \left(\begin{array}{l} 2s \Leftarrow LS \Rightarrow L = 2 \\ 15 \end{array} \right)$$

$$\begin{array}{c} 4s^3 + 10s^1 \\) s^7 + 9s^2 + 3 \\ - s^7 - \frac{10}{4}s^2 \\ \hline \end{array} \quad \left(\begin{array}{l} 15 \\ 7 \end{array} \right)$$

5- Quotient so must contain 5 elements in Cauer I form.

$$\begin{array}{c} \frac{3}{2}s^2 + 3 \\) 9s^3 + 10s^1 \\ - 9s^3 - 8s^1 \\ \hline \end{array} \quad \left(\begin{array}{l} 2s \times x \\ 3 \end{array} \right)$$

$$\begin{array}{c} 2H \quad 8/3H \quad 2/3H \\ \hline \text{errr} & \text{errr} & \text{errr} \\ \hline \frac{1}{4}F & \frac{3}{4}F \\ \hline \end{array}$$

Hg. Cauer I form.

$$\begin{array}{c} 2s \quad \frac{3}{2}s^2 + 3 \quad \left(\frac{3}{2}s \times \frac{1}{2} \right) \\ \hline \frac{5}{2}s^2 \\ \hline 3 \quad 2s \quad \left(\frac{2s}{3} \right) \\ \hline x \end{array}$$

Cauer II. Arrange the polynomials in the ascending order.

$$g \cdot 2(s) = \frac{(s^2+1)(s^2+3)}{s(s^2+2)}$$

$$2(s) = \frac{s^4 + 4s^2 + 3}{s^3 + 2s}$$

now continue fraction.

$$\frac{1}{2s+s^3} \left| \begin{array}{l} 3+4s^2+s^4 \\ \hline s+\frac{3s^2}{2} \end{array} \right. \text{ capacitor. } \frac{1}{cs} = \frac{1}{\frac{2}{3}s} \\ C = \frac{2}{3}$$

$$\frac{5s^2+s^4}{2} \left| \begin{array}{l} 2s+s^3 \\ \hline 2s+\frac{4s^3}{5} \end{array} \right. \frac{2 \times 2}{s+5} = \frac{1}{5s} \\ 4$$

$$\frac{s^3}{5} \left| \begin{array}{l} \frac{5}{2}s^2+s^4 \\ \hline \frac{5}{2}s^2 \end{array} \right. \frac{5 \times 5}{2s} = \frac{1}{2s} \\ 25$$

$$s^8 \left| \begin{array}{l} \frac{s^3}{5} \\ \hline s^3 \end{array} \right. \frac{1}{s \times 5} = \frac{1}{5s} \\ 1$$

②

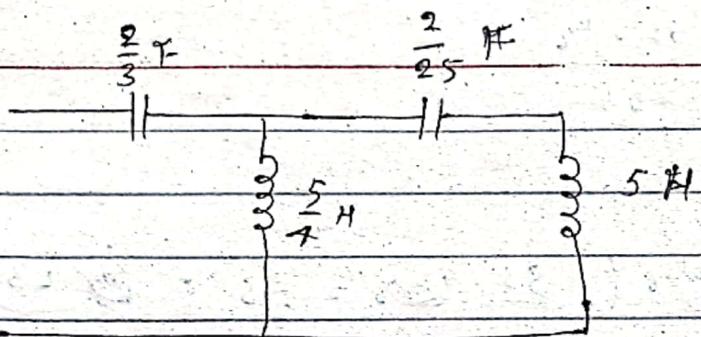


fig. causal II form.

Note: Cauer I \rightarrow Descending order
 Cauer II \rightarrow Ascending order

$$(i) Z(s) = \frac{6s^3 + 2s}{9s^2 + 4s^2 + 1/6} \quad \text{25/10/13}$$

Find the first cauer networks.

$$\frac{6s^3 + 2s}{9s^2 + 4s^2 + 1/6} = \frac{6s^3 + 2s}{\cancel{9s^2 + 4s^2} + \frac{1}{6}} \quad \left(\frac{6}{9}s \right)$$

since the order of denominator is greater than the numerator polynomial, we have to invert the given function and proceed with the continue fraction.

$$\text{Invert} \Rightarrow \frac{1}{Z(s)} = \frac{9s^4 + 9s^2 + 1/6}{6s^3 + 9s}$$

continued fraction

$$6s^3 + 2s \left(9s^9 + 9s^2 + 16 \right) . \frac{9s}{6} = 2s = \frac{3}{2}s = L(s)$$

$$\left(s^2 + \frac{1}{6} \right) 6s^3 + 2s \quad \left(6s^3 + s \right)$$

plate:

plate! $s^2 + \frac{1}{16}$ (s)
invert $\frac{9}{16}$ gives fraction $\frac{1}{9}$

invert each terms fraction will



प्रारंभिक अवस्था element एक्सेस

Growth ការបន្ថែម

$$= \frac{s^2}{16} s \left(\frac{6s}{s} \right)$$

Cancer I.

Normal cat:

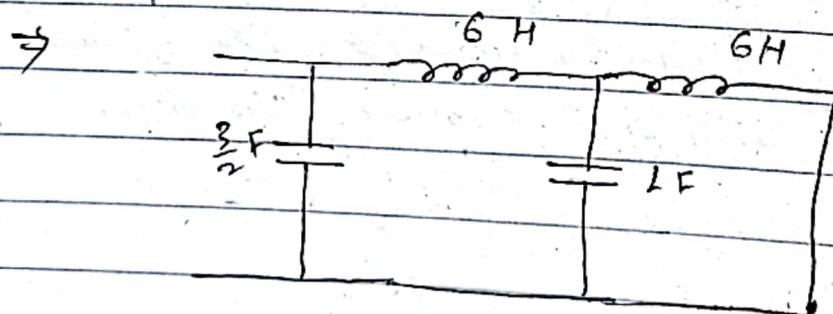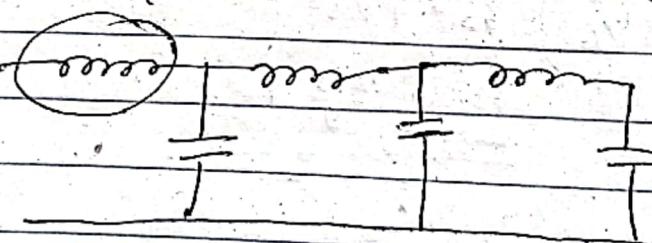

Cauer II

obtain the Cauer II for the given function.

$$Z(s) = \frac{8s^3 + 3s}{2s^4 + 10s^2 + 3}$$

=)

inverting, $\frac{1}{Z(s)} = \frac{2s^4 + 10s^2 + 3}{8s^3 + 3s} = \frac{3 + 10s^2 + 2s^4}{3s + 8s^3}$

$$\frac{3s + 8s^3}{3 + 10s^2 + 2s^4} \left(\frac{1}{s} \right) = \frac{1}{cs}$$


$$\frac{3 + 8s^2}{2s^2 + 2s^4} \left(\frac{3}{2s} \right) = \frac{3}{2s}$$

$$\frac{5s^3}{2s^2 + 2s^4} \left(\frac{2}{5s} \right) = \frac{2}{5s}$$


$$\frac{2s^4}{5s^3} \left(\frac{5}{2s} \right) = \frac{5}{2s}$$

$$= \cancel{\frac{5}{2s}}$$

+ remove

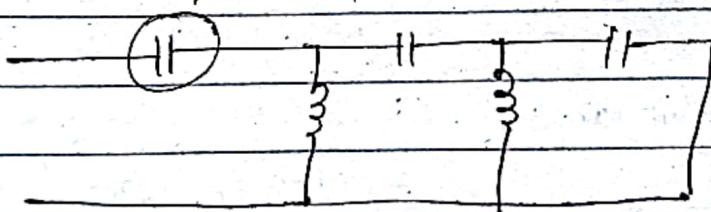

so on =>

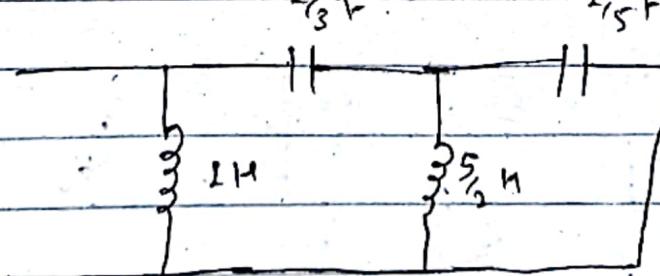

RC Impedance or RL Admittance network.


Properties:

1. Poles and zeros lie on the negative real axis and they are in alternative form.
2. The singularity nearest to (or at) the origin must be a pole whereas the singularity nearest to (or at) the infinity is a zero.
3. The residue of the poles must be real and positive.

* Foster Ist form of RC impedance


$$\text{let } Z(s) = k_0 + \frac{k_1}{s + \sigma_1} + \frac{k_2}{s + \sigma_2} + \frac{k_3}{s + \sigma_3} + \dots + \frac{1}{s + \sigma_{\infty}} \text{ is}$$

The partial fraction.

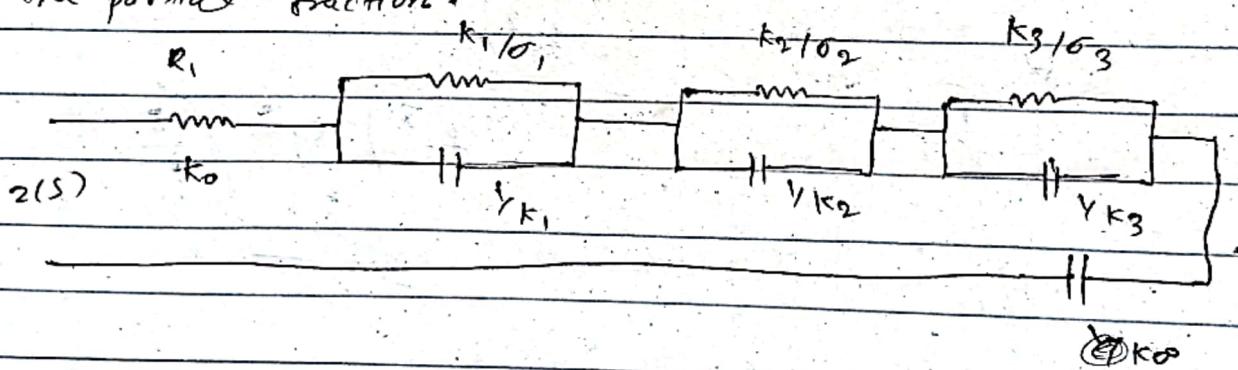


* Foster IInd form (from admittance)
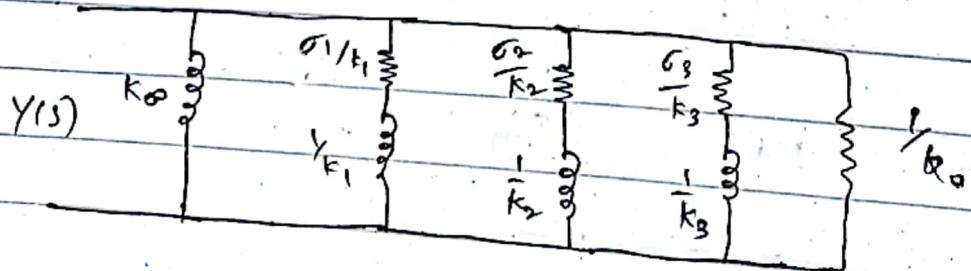
$$\text{let } Y(s) = k_0 + \frac{k_1}{s + \sigma_1} + \frac{k_2}{s + \sigma_2} + \dots + \frac{1}{s + \sigma_{\infty}} \text{ is the partial fraction.}$$




* Cauer Ist form

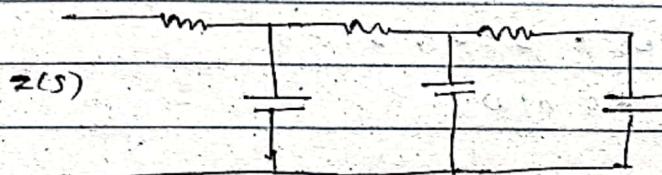If the function is an impedance function (continued fraction method)




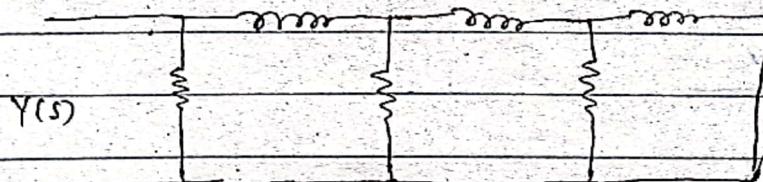But if the function is an admittance function




* Cauer IInd form

If impedance

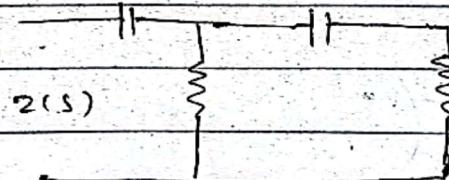

If admittance,

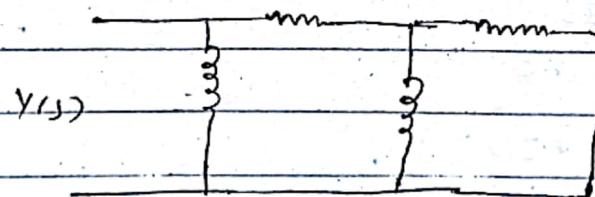

Q. obtain the Foster I and Foster II form of the given function.

$$8(s+2)(s+9)$$

$$F(s) = \frac{s(s+3)}{}$$

Poles $\neq s=0, s=-3$

RC network

(i) For Foster I.

assume $F(s)$ as impedance

(Rule: denominator power should higher than numerator)

$$F(s) = \frac{s(s+2)(s+9)}{s(s+3)}$$

$$= \frac{3(s^2 + 6s + 18)}{s^2 + 3s}$$

$$= \frac{3s^2 + 18s + 27}{s^2 + 3s}$$

$$\begin{array}{r} s^2 + 3s \\) 3s^2 + 18s + 27 \\ - 3s^2 - 9s \\ \hline 9s + 27 \end{array}$$

$$F(s) = 8 + \frac{9s + 27}{s^2 + 3s}$$

$$= 8 + \frac{9s + 27}{s(s+3)}$$

$$\frac{9s + 27}{s(s+3)} = \frac{A}{s} + \frac{B}{s+3}$$

$$A = \left. \frac{9s+24}{s+3} \right|_{s=0}$$

= 8

$$B = \left. \frac{9s+24}{s} \right|_{s+3=0}$$


$s = -3$

$$= \frac{9(-3)+24}{-3}$$

= 1

$$F(s) = 3 + \frac{8}{s} + \frac{1}{s+3} = k_0 + \frac{1}{s+3} + \frac{k_1}{s+\sigma_1}$$


Foster I form,

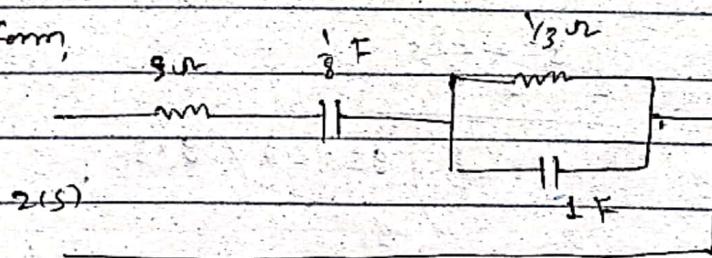

(ii) For foster II

assume $F(s)$ as admittance.

$$F(s) = 3 + \frac{8}{s} + \frac{1}{s+3}$$

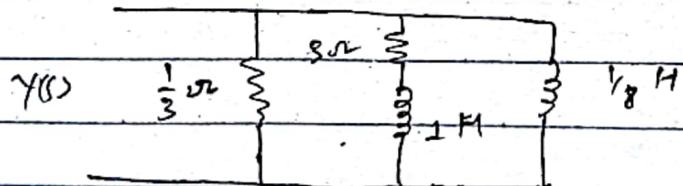

* Cauer I.

$$Z(s) = \frac{3(s+2)(s+9)}{s(s+3)} = \frac{3s^2 + 18s + 27}{s^2 + 3s} \quad (\text{decreasing order})$$

$$\begin{array}{r} s^2 + 3s \\ \times 3s^2 + 18s + 27 \\ \hline 9s^2 + 9s \end{array}$$

$$\begin{array}{r} s^2 + 3s \\ \times 9s + 27 \\ \hline s^2 + \frac{27}{9}s \end{array}$$


$$\begin{array}{r} s \\ \times 9s + 27 \\ \hline -9s \end{array}$$

$$\begin{array}{r} s \\ \times 27 \\ \hline -27 \end{array}$$

3s²

27s²

$\frac{s}{3}$

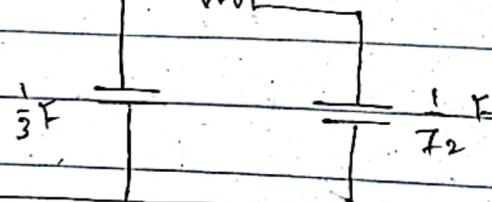

$$\# \quad z(s) = \frac{6s^3 + 2s}{s^2 + 4s + 3} \quad (\text{2013 spring})$$

Realize the following RC driving point impedance function
 in (i) Foster I form and in
 (ii) Cauer I form

$$y(s) = \frac{s^2 + 6s + 8}{s^2 + 4s + 3}$$

$$= \frac{(s+2)(s+4)}{(s+1)(s+3)}$$

For Foster I form (partial fraction)

since the highest power of numerator and denominator are equal.

$$\begin{array}{r} s^2 + 6s + 8 \\ s^2 + 4s + 3 \\ \hline 2s + 5 \end{array}$$

$$y(s) = 1 + \frac{2s+5}{s^2 + 4s + 3}$$

$$= 1 + \frac{2s+5}{(s+1)(s+3)}$$

$$\frac{2s+5}{(s+1)(s+3)} = \frac{A}{s+1} + \frac{B}{s+3} \quad B = \frac{2s+5}{s+1} \Big|_{s+3=0}$$

$$A = \frac{2s+5}{s+3} \Big|_{s+1=0} \quad s=-1 \quad = \frac{-6+5}{-3+1} = -\frac{1}{2}$$

$$= \frac{-2+5}{-1+3} = \frac{3}{2}$$

$$g(s) = L + \frac{3}{s+1} + \frac{4}{s+3}$$

Foster 5 form.

For cancer: I form (citrine fraction)

$$g(s) = \frac{s^2 + 6s + 8}{s^2 + 9s + 3} \quad (\text{Descending order})$$

$$\begin{array}{r} s^2 + 9s + 3 \\ \times s^2 + 6s + 8 \\ \hline s^2 + 9s + 3 \\ \hline 9s + 5) s^2 + 9s + 3 \end{array}$$

$$\left(\frac{3s+3}{2} \right)^{2s+5} \left(\frac{4}{3} \right)$$

$$2\pi \quad q_3 \omega \quad \frac{1}{3} \omega \quad 25 + 8$$

cancer I form.

$$3) k \left(\begin{array}{c} 1 \\ 3 \\ -1 \end{array} \right)$$

RL Impedance / RC Admittance Ckt.

- Opposite of Re impedance. (near the origin zero instead of poles)


& Foster I of RL (Partial fraction)

$$\text{Let } Z(s) = k_0 + \frac{k_0 s}{s} + \frac{k_1}{s + \sigma_1} + \frac{k_2}{s + \sigma_2} + \dots$$

$$\frac{Z(s)}{s} = k_0 + \frac{k_0}{s} + \frac{k_1}{s + \sigma_1} + \frac{k_2}{s + \sigma_2} + \dots$$


Partial factoring
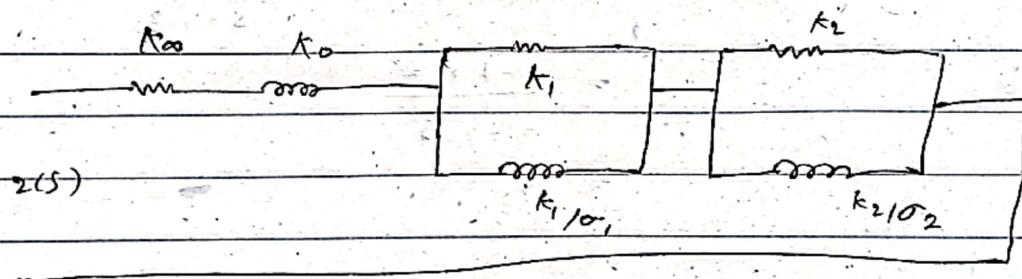
$$Z(s) = k_0 s + k_0 + \frac{k_1 s}{s + \sigma_1} + \frac{k_2 s}{s + \sigma_2} + \frac{k_3 s}{s + \sigma_3} + \dots$$



$$\text{Foster II. } Y(s) = k_0 s + k_0 + \frac{k_1 s}{s + \sigma_1} + \frac{k_2 s}{s + \sigma_2} + \dots$$

(admittance):

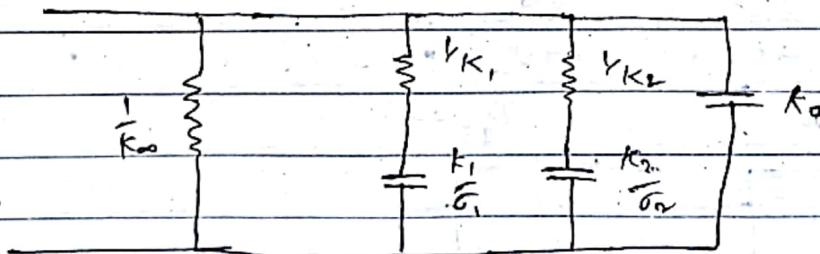

2015 spring.

Synthesizes into Foster I and Cauer II forms of RC driving function.

$$Z_{RC} = \frac{(s+1)(s+9)}{s(s+2)(s+5)}$$

∴

Foster I form:


$$Z_{RC} = \frac{A}{s} + \frac{B}{s+2} + \frac{C}{s+5}$$

$$A = \frac{(s+1)(s+9)}{(s+2)(s+5)} \Big|_{s=0} = \frac{4}{10} = \frac{2}{5}$$

$$B = \frac{(s+1)(s+9)}{s(s+2)(s+5)} \Big|_{s+2=0} = \frac{-2 \times 8}{-2+3} = -16$$

$$C = \frac{(s+1)(s+9)}{s(s+5)} \Big|_{s+5=0} = \frac{-4 \times -1}{-5+3} = \frac{4}{15}$$
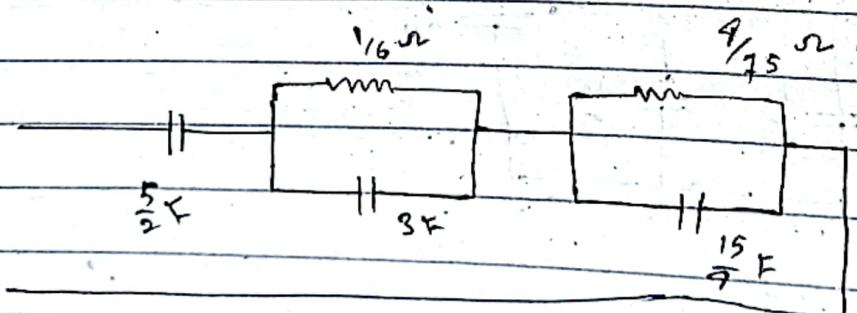
$$Z_{RC} = \frac{2/5}{s} + \frac{4/15}{s+2} + \frac{4/15}{s+5}$$



Foster I form.

Cauer II form:

$$= \frac{(s+1)(s+9)}{s(s+2)(s+5)} = \frac{s^2 + 8s + 9}{s(s^2 + 7s + 10)} = \frac{s^2 + 8s + 9}{s^3 + 7s^2 + 10s}$$

Arrange in ascending order;

$$= \frac{4 + 8s + s^2}{10s + 7s^2 + s^3}$$

$$\left(10s + 7s^2 + s^3 \right) \left(4 + 8s + s^2 \right) \left(\frac{4}{10s} \right)$$
$$x + \frac{28}{10}s + \frac{9s^2}{10}$$

$$\left(\frac{11}{5} \frac{28}{10}s + \frac{5}{10}s^2 \right) \left(10s + 7s^2 + s^3 \right) \left(\frac{2}{11} \right)$$
$$10s + \frac{6s^2}{55}$$

$$\left(\frac{879}{55} s^2 + s^3 \right) \left(\frac{11}{5} s + \frac{3}{5} s^3 \right)$$

RL Impedance (s)


Properties:

1. Poles and zeros are located on the negative real axis.
2. The singularity nearest to the origin is a zero and the singularity nearest to (or at) the infinity is a pole.
3. The residue of the poles must be real and true.

Rule for Foster I and II


$\frac{Z(s)}{s}$. start with dividing $Z(j)$ or $X(s)$ by s .
or multiply right side by s

Cauer I, for Z_L

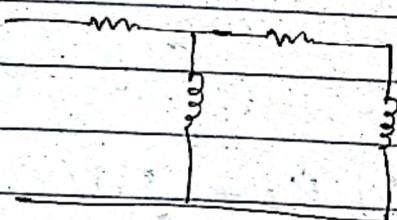

RL impedance can be synthesised for Cauer I

Cauer II for Z_L

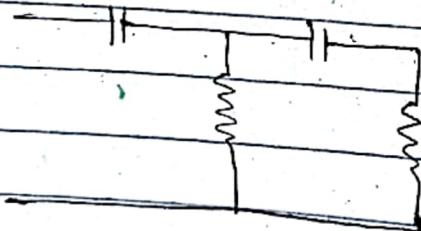

RL admittance can be synthesised for Cauer II

q. Obtain the factor forms for the given impedance function.

$$Z(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$

Factor I:

$$\frac{Z(s)}{s} = \frac{2(s+1)(s+3)}{s(s+2)(s+6)}$$

$$\frac{Z(s)}{s} = \frac{A}{s} + \frac{B}{s+2} + \frac{C}{s+6}$$

$$A = \left. \frac{2(s+1)(s+3)}{(s+2)(s+6)} \right|_{s=0} \quad B = \left. \frac{2(s+1)(s+3)}{s(s+6)} \right|_{s=-2}$$

$$= \frac{2+1 \times 3}{2+6} = \frac{2+3}{8} = \frac{5}{8}$$

$$= \frac{2 \times -1 \times 1}{-2 \times 6} = \frac{-2 \times 1}{-12} = \frac{1}{6}$$

$$= \frac{1}{2}$$

$$C = \left. \frac{2(s+1)(s+3)}{s(s+2)} \right|_{s=-6}$$

$$= \frac{2 \times -5 \times -3}{-5 \times -4} = \frac{30}{20} = \frac{3}{2}$$


$$= \frac{-6 \times -8 \times 2}{2} = \frac{96}{2} = 48$$

$$= \frac{5}{8}$$

$$\frac{Z(s)}{s} = \frac{\frac{1}{2}}{s} + \frac{\frac{1}{6}}{s+2} + \frac{\frac{5}{8}}{s+6}$$

$$Z(s) = \frac{\frac{1}{2}}{s} + \frac{\frac{1}{6}s}{s+2} + \frac{\frac{5}{8}s}{s+6}$$

$$= R_0 + \frac{k_1 s}{s+\omega_1} + \frac{k_2 s}{s+\omega_2}$$

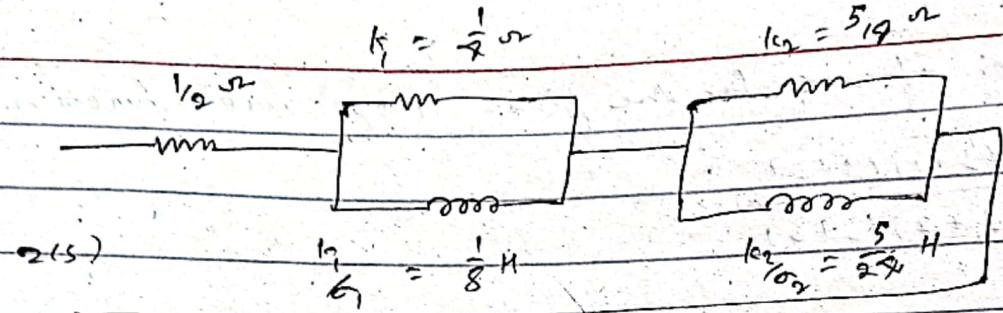

Foster II:

$$Y(s) = \frac{(s+2)(s+6)}{2(s+1)(s+3)}$$

$$\frac{Y(s)}{s} = \frac{0.5(s+2)(s+6)}{s(s+1)(s+3)} = \frac{A}{s} + \frac{B}{s+1} + \frac{C}{s+3}$$

$$A = \frac{0.5(s+2)(s+6)}{(s+1)(s+3)} \Big|_{s=0} = \frac{0.5 \times 2 \times 6}{2 \times 3} = 1 \times 8$$

$$= 2.$$

$$C = \frac{0.5(s+2)(s+6)}{s(s+1)} \Big|_{s=-3} = \frac{0.5 \times -1 \times 8}{-3 \times -2} = -\frac{1}{3}$$

Here residue of poles are negative so we cannot synthesized. Foster III

$$B = \frac{0.5(s+2)(s+6)}{s(s+3)} \Big|_{s=-1} = -\frac{1}{2}$$

$$= \frac{0.5 \times 1 \times 5}{-1 \times 2} = -\frac{5}{4}$$

$$= -\frac{5}{4}$$